

**CSE 664 Introduction to System-on-Chip Design**  
**Final Project – 8-Bit Microcontroller**



Revision: 1.0

Date Prepared: June 2023

Prepared by: Austin Benedetti, Daniel Ems, Nicholas Lyons, Mike Pena, Trent Reeves, Mimansa Verma, Derrick Ward, Jiawen Zhen

Prepared for: CSE 664 Introduction to System-on-Chip Design, Spring 2023,  
section M401, Professor Mohammed Abdallah



## Contents

|       |   |    |
|-------|---|----|
| 1     | Design Documentation.....                         | 4  |
| 1.1   | Entity: acc_simple .....                          | 4  |
| 1.1.1 | Diagram.....                                      | 4  |
| 1.1.2 | Description.....                                  | 4  |
| 1.1.3 | Ports.....  | 4  |
| 1.1.4 | Signals .....                                     | 5  |
| 1.1.5 | Processes.....                                    | 5  |
| 1.2   | Entity: ALU_8bit .....                            | 6  |
| 1.2.1 | Diagram.....                                      | 6  |
| 1.2.2 | Description.....                                  | 6  |
| 1.2.3 | Ports .....                                       | 6  |
| 1.2.4 | Processes.....                                    | 6  |
| 2     | Entity: controller_fsm .....                      | 8  |
| 2.1   | Diagram.....                                      | 8  |
| 2.2   | Description.....                                  | 8  |
| 2.3   | Ports .....                                       | 8  |
| 2.4   | Processes.....                                    | 9  |
| 3     | Entity: nbit_two_one_mux.....                     | 10 |
| 3.1   | Diagram.....                                      | 10 |
| 3.2   | Description.....                                  | 10 |
| 3.3   | Ports .....                                       | 10 |
| 4     | Simulations .....                                 | 11 |
| 4.1   | Modelsim - accumulator.v .....                    | 11 |
| 4.2   | Modelsim – ALU_8bit.v.....                        | 11 |
| 4.3   | Modelsim – controller_fsm.v .....                 | 12 |
| 4.4   | Modelsim – nbit_two_one_mux.v.....                | 12 |
| 4.5   | Modelsim – program_counter.v .....                | 12 |
| 5     | References.....                                   | 13 |
|       | APPENDIX A: 8-Bit Microcontroller Code Base ..... | 13 |




THIS PAGE INTENTIONALLY LEFT BLANK

## 1 Design Documentation

### 1.1 Entity: acc\_simple

- **File:** accumulator.v

#### 1.1.1 Diagram

 

#### 1.1.2 Description

A register in which intermediate arithmetic logic unit results are stored. This simple 8-bit accumulator's output will continuously grow by increments of the input until reset.

Note - Overflow is not handled

#### 1.1.3 Ports

| Port name | Direction | Type    | Description                                 |
|-----------|-----------|---------|---|
| clock     | input     |         | Clock. Output is posedge triggered          |
| reset     | input     |         | Clears register value (1 = clear, 0 = hold) |
| in        | input     | [7 : 0] | Input from ALU                              |
| out       | output    | [7 : 0] | Output return to ALU                        |



#### 1.1.4 Signals

---

| Name        | Type        | Description                              |
|-------------|-------------|--|
| accumulator | reg [7 : 0] | Temporary storage for accumulator output |

#### 1.1.5 Processes

---

- unnamed: ( @(posedge clock or posedge reset) )

**Type:** always


**Description**

Increments output by input at rising edge of clock.  
If reset is high then clear output.

## 1.2 Entity: ALU\_8bit

- File: ALU\_8bit.v

### 1.2.1 Diagram

 

### 1.2.2 Description

A combinational digital circuit that performs arithmetic and bitwise operations on integer binary numbers.

### 1.2.3 Ports

| Port name     | Direction | Type  | Description  |
|---------------|-----------|-------|--|
| alu_out       | output    | [7:0] | 8 bit result (connected to mux that is connected to ACC) |
| alu_zero_flag | output    |       | Set if result is zero (connected to controller)          |
| alu_carry_out | output    |       | Set if carry bit is needed (connected to controller)     |
| alu_select    | input     | [3:0] | Select ALU operation (received from controller)          |
| alu_a_in      | input     | [7:0] | ACC ALU input  |
| alu_b_in      | input     | [7:0] | REG ALU input  |

### 1.2.4 Processes

- unnamed: ( @(alu\_a\_in or alu\_b\_in or alu\_select) )



**Type:** always


**Description**

The ALU outputs change anytime the inputs change (combinational logic).

## 2 Entity: controller\_fsm

- File: controller\_fsm.v

### 2.1 Diagram

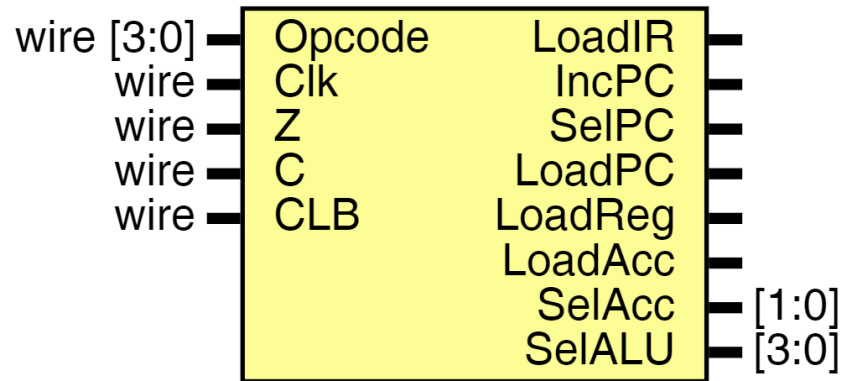

### 2.2 Description

Model that uses a known set of inputs to define several combinations of outputs and states.

### 2.3 Ports

| Port name | Direction | Type | Description   |
|-----------|-----------|------|---|
| LoadIR    | output    |      | Load instruction register with next instruction - (Should be checked before update) |
| IncPC     | output    |      | Program counter which is incremented only to next instruction                       |
| SelPC     | output    |      | Used to increment PC by immediate or val in reg                                     |
| LoadPC    | output    |      | Signal to update PC value - (Should be checked before JUMP ONLY)                    |





| Port name | Direction | Type       | Description  |
|-----------|-----------|------------|--|
| LoadReg   | output    |            | Signal to update register - (Should be checked before update)            |
| LoadAcc   | output    |            | Signal to update accumulator - (Should be checked before update)         |
| SelAcc    | output    | [1:0]      | Select signal for ACC muxes - (SelAcc[1] = SelAcc1, SelAcc[0] = SelAcc0) |
| SelALU    | output    | [3:0]      | Select signal for ALU operation (opcode)                                 |
| Opcode    | input     | wire [3:0] | Opcode from instruction register   |
| Clk       | input     | wire       | Clock signal   |
| Z         | input     | wire       | Zero bit   |
| C         | input     | wire       | Carry bit  |
| CLB       | input     | wire       | TODO: WHAT IS THIS?  |

## 2.4 Processes

- unnamed: ( @(Clk) )

**Type:** always


**Description**

Case statement for setting control signals

### 3 Entity: nbit\_two\_one\_mux

- **File:** nbit\_two\_one\_mux.v

#### 3.1 Diagram

 

#### 3.2 Description


A data selector device that selects between several analog or digital input signals and forwards the selected input to a single output line.

#### 3.3 Ports



| Port name | Direction | Type                 | Description          |
|-----------|-----------|----------------------|----------------------|
| A_WIDTH   | input     | parameter            |                      |
| B_WIDTH   | input     | parameter            | Width of INPUT BUS A |
| OUT_WIDTH | input     | parameter            | Width of INPUT BUS B |
| bus_out   | output    | wire [OUT_WIDTH-1:0] | Output bus           |
| bus_a     | input     | wire [A_WIDTH-1:0]   | Input bus A          |
| bus_b     | input     | wire [B_WIDTH-1:0]   | Input bus B          |
| select    | input     | wire                 | Select Signal        |


## 4 Simulations

### 4.1 Modelsim - accumulator.v

 


### 4.2 Modelsim – ALU\_8bit.v

  


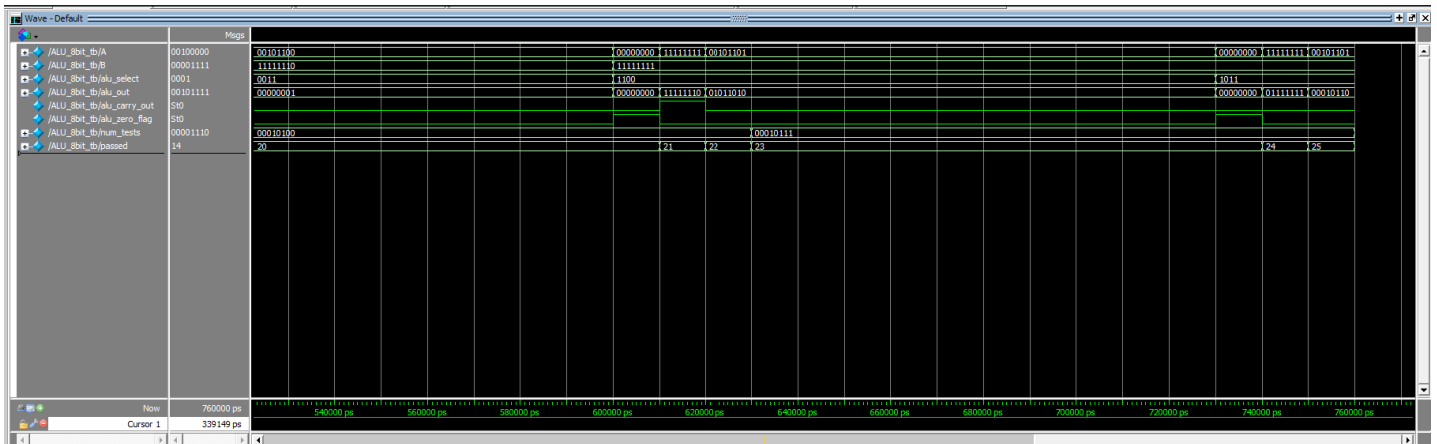


### 4.3 Modelsim – controller\_fsm.v

 

### 4.4 Modelsim – nbit\_two\_one\_mux.v

 

### 4.5 Modelsim – program\_counter.v

 



## **5 References**

### **APPENDIX A:**

#### **8-Bit Microcontroller Code Base**



Prepared by:

Austin Benedetti, Daniel Ems, Nicholas Lyons, Mike Pena, Trent Reeves, Mimansa Verma,  
Derrick Ward, Jiawen Zhen